



# Electronic Circuits Design

---


## *Lecture – 12*

- *Decoder*
- *Multiplexer*
- *Flip-Flop*



***Yeonbae Chung***  
***School of Electronics Engineering***  
***Kyungpook National University***



EN	A	B	C	D0	D1	D2	• • •	D7
0	X	X	X	0	0	0		0
1	0	0	0	1	0	0		0
1	0	0	1	0	1	0		0
1	0	1	0	0	0	1		0
	•					•		
	•					•		
	•					•		
1	1	1	1	0	0	0		1

 

### 3-to-8 Decoder

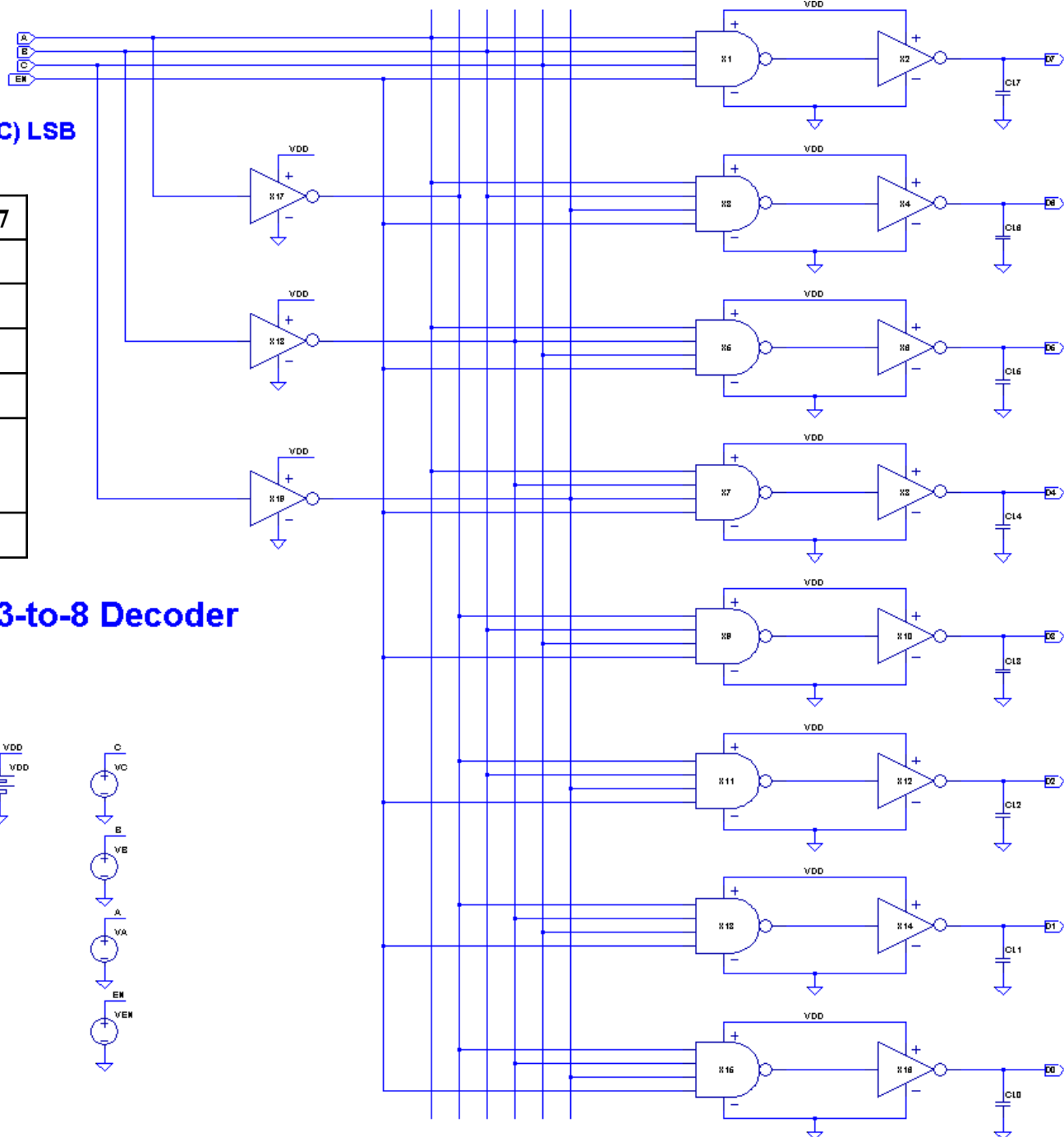 




## **Lab-1: 3-to-8 Decoder**


### ❖ **Simulation Condition**

- CMOS model parameter: MOSIS/TSMC\_0.18 $\mu$ m ( $L_P = L_N = 0.18\mu$ m)
- VDD = 1.8 V, CL0 = CL1 = CL2 =  $\dots$  = CL7 = 200fF
- VC = PULSE(0 1.8V 4.5ns 0.5ns 0.5ns 4.5ns 10ns)
- VB = PULSE(0 1.8V 9.5ns 0.5ns 0.5ns 9.5ns 20ns)
- VA = PULSE(0 1.8V 19.5ns 0.5ns 0.5ns 19.5ns 40ns)
- VEN = PULSE(0 1.8V 39.5ns 0.5ns 0.5ns 39.5ns 80ns)
- Transient analysis from 0 to 200 ns

- 1) Create the LTSpice schematic of the 3-to-8 decoder.
- 2) Assuming  $\mu_N = 2.5\mu_P$ , determine transistor sizes of each gate to provide  $t_{pLH}$  and  $t_{pHL}$  less than 300 ps.
- 3) Obtain a plot of A, B, C, EN, D0, D1, D2, D3, D4, D5, D6 and D7 versus time.
- 4) Measure the average active power consumed by the decoder.
- 5) Change the supply voltage to 0.9 V, then obtain the average active power consumed by the decoder. What percent is it reduced compared to VDD = 1.8 V ?

# 4-to-1 Multiplexer

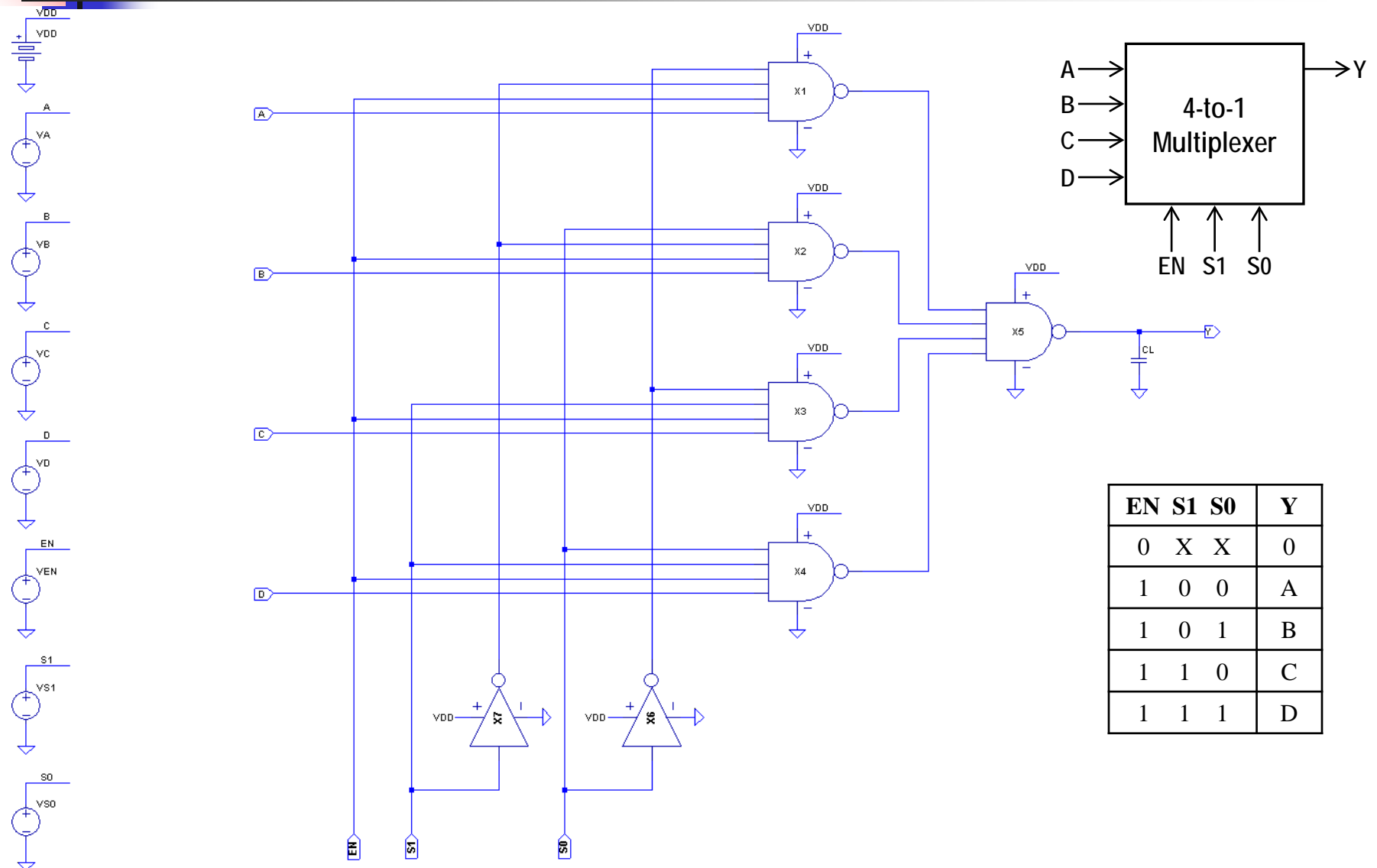

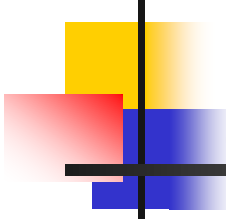




## **Lab-2: 4-to-1 Multiplexer**

### ❖ **Simulation Condition**

- CMOS model parameter: MOSIS/TSMC\_0.18 $\mu$ m ( $L_P = L_N = 0.18\mu$ m)
- VDD = 1.2 V, CL = 50fF
- VA = PULSE(0 1.2V 2ns 0.5ns 0.5ns 2ns 5ns)
- VB = PULSE(0 1.2V 4.5ns 0.5ns 0.5ns 4.5ns 10ns)
- VC = PULSE(0 1.2V 9.5ns 0.5ns 0.5ns 9.5ns 20ns)
- VD = PULSE(0 1.2V 19.5ns 0.5ns 0.5ns 19.5ns 40ns)
- VEN = PWL(0 0V 161.25ns 0V 161.75ns 1.2V 481.75ns 1.2V 482.25ns 0V)
- VS1 = PULSE(0 1.2V 79.5ns 0.5ns 0.5ns 79.5ns 160ns)
- VS0 = PULSE(0 1.2V 39.5ns 0.5ns 0.5ns 39.5ns 80ns)
- Transient analysis from 0 to 640 ns


- 1) Create the LTSpice schematic of the 4-to-1 multiplexer.
- 2) Assuming  $\mu_N = 2.5\mu_P$ , determine transistor sizes of each gate to provide  $t_{pLH}$  and  $t_{pHL}$  less than 300 ps.
- 3) Obtain a plot of A, B, C, D, EN, S1, S0 and Y versus time.
- 4) Verify the logic functionality.

# Positive-Edge Triggered D Flip-Flop

  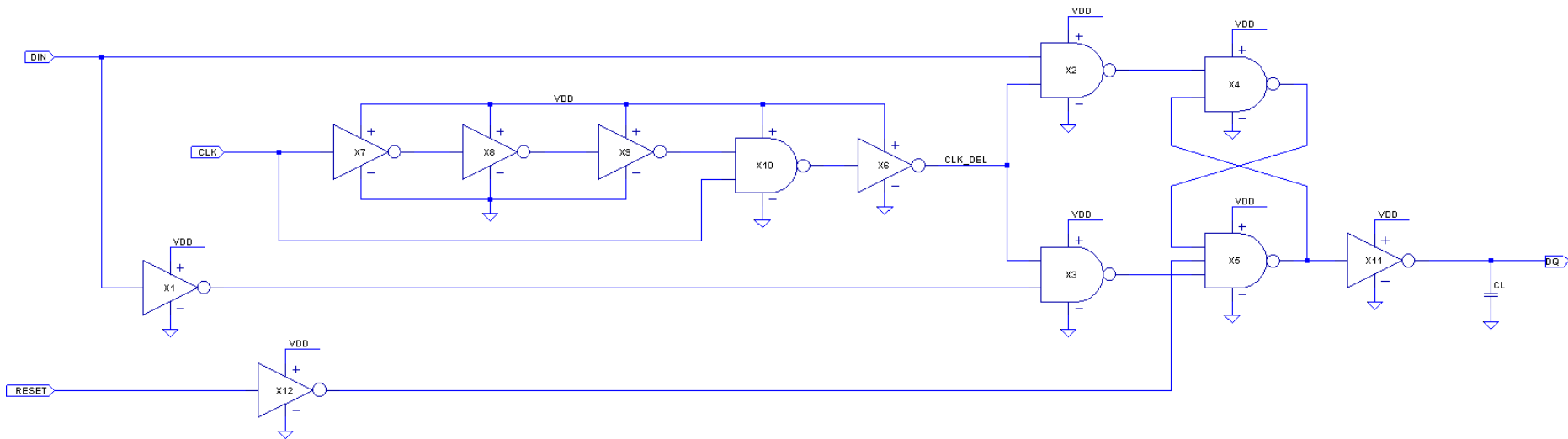

RESET	DIN	CLK	DQ
H	X	X	L
L	L	↑	L
L	H	↑	H

# Flip-Flop Timing Parameters

 

- $T_{\text{setup}}$ : the length of time that the incoming data must be stable before the clock arrives for proper operation
- $T_{\text{hold}}$ : the length of time that the data must remain stable after the clock arrives for proper operation
- $T_{\text{CLK-Q}}$ : the delay time from CLK to Q transition



## ***Lab-3: Positive-Edge Triggered D Flip-Flop***

### ❖ **Simulation Condition**

- CMOS model parameter: MOSIS/TSMC\_0.18 $\mu$ m
- VDD = 1.8 V, CL = 100fF
- Inverter chain (X7, X8, X9):  $W_P/L_P = 3.8\mu\text{m}/0.5\mu\text{m}$ ,  $W_N/L_N = 1\mu\text{m}/0.5\mu\text{m}$
- Inverter (X1, X6, X11, X12):  $W_P/L_P = 1.5\mu\text{m}/0.18\mu\text{m}$ ,  $W_N/L_N = 0.6\mu\text{m}/0.18\mu\text{m}$
- 2-input NAND (X2, X3, X4, X10):  $W_P/L_P = 1.5\mu\text{m}/0.18\mu\text{m}$ ,  $W_N/L_N = 1.2\mu\text{m}/0.18\mu\text{m}$
- 3-input NAND (X5):  $W_P/L_P = 1.5\mu\text{m}/0.18\mu\text{m}$ ,  $W_N/L_N = 1.8\mu\text{m}/0.18\mu\text{m}$
- VCLK = PULSE(0 1.8V 6.5ns 0.5ns 0.5ns 4.5ns 10ns)
- VDIN = PULSE(0 1.8V 4.5ns 0.5ns 0.5ns 8.5ns 20ns)
- VRESET = PULSE(1.8V 0 2.5ns 0.5ns 0.5ns 47.5ns 100ns)
- Transient analysis from 0 to 80 ns

- 1) Create the LTSpice schematic of the positive-edge triggered D flip-flop.
- 2) Obtain a plot of RESET, DIN, CLK, CLK\_DEL and DQ versus time.
- 3) Verify the logic functionality.
- 4) Measure  $T_{CLK-Q}$ .
- 5) Make comments if you need.