



# Electronic Circuits Design


---

## *Lecture – 4*

- *Summing Amplifier*
- *Differential Amplifier*
- *Instrumentation Amplifier*

***Yeonbae Chung***  
***School of Electronics Engineering***  
***Kyungpook National University***

# Summing Amplifier

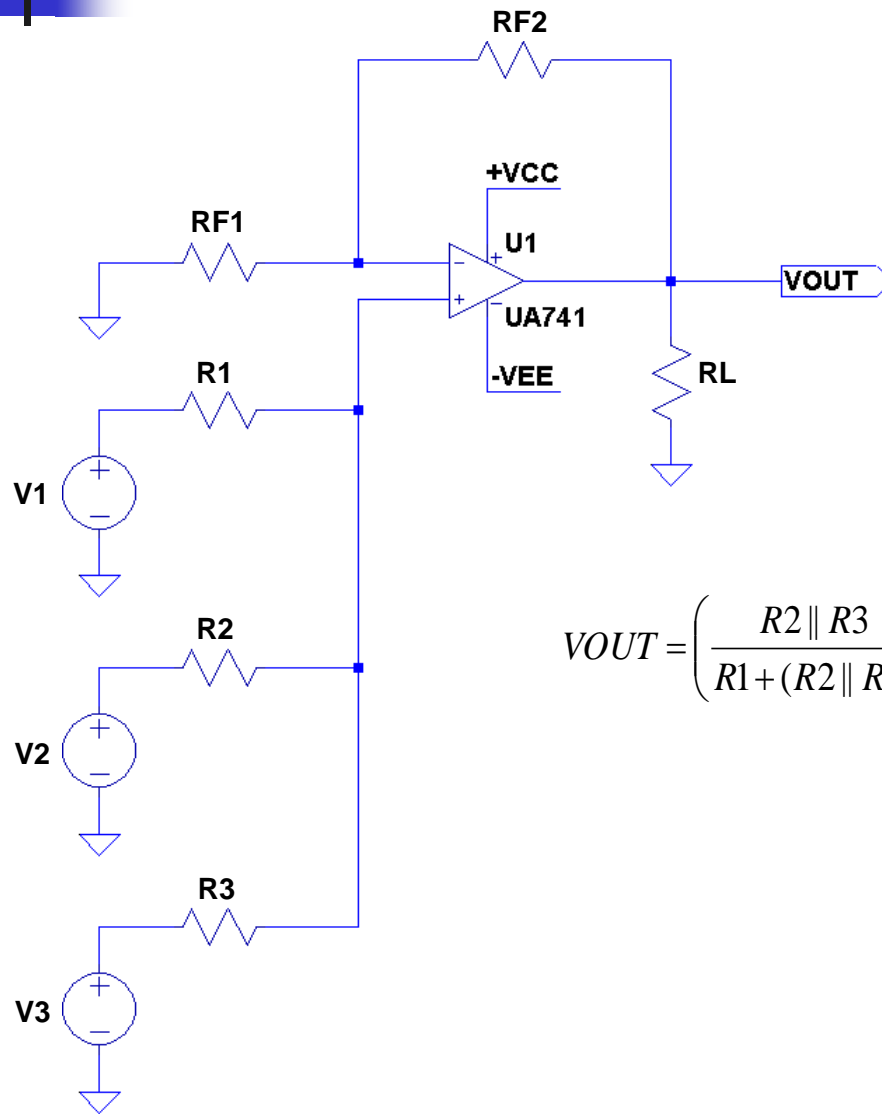

$$V_{OUT} = \left( \frac{R2 \parallel R3}{R1 + (R2 \parallel R3)} V1 + \frac{R1 \parallel R3}{R2 + (R1 \parallel R3)} V2 + \frac{R1 \parallel R2}{R3 + (R1 \parallel R2)} V3 \right) \left( 1 + \frac{RF2}{RF1} \right)$$




## ***Lab-1: Summing Amplifier***

### **❖ Simulation Condition**

- Op Amp:  $\mu A741$
- $R_L = 5\text{ k}\Omega$
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$
- $V_1 = 1\sin(2\pi \times 10^3 t)\text{ V}$ ,  $V_2 = 2\sin(2\pi \times 10^3 t)\text{ V}$ ,  $V_3 = 3\sin(2\pi \times 10^3 t)\text{ V}$
- Transient analysis from 0 to 10ms

- 1) Determine the values of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_{F1}$  and  $R_{F2}$  to provide  $V_{OUT} = V_1 + V_2 + V_3$ .
- 2) Create the LTSpice schematic of the summing amplifier circuit.
- 3) Obtain a plot of  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_{OUT}$  versus time.
- 4) Change the input voltages to  $V_1 = 1\sin(2\pi \times 400 t)\text{ V}$ ,  $V_2 = 1\sin(2\pi \times 2000 t)\text{ V}$  and  $V_3 = 1\sin(2\pi \times 10^4 t)\text{ V}$ , then obtain a plot of  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_{OUT}$  versus time.
- 5) Change the input voltages to  $V_1 = \text{PULSE}(0\text{V } 2\text{V } 2\text{ms } 1\text{ns } 1\text{ns } 1.95\text{ms } 4\text{ms})$ ,  $V_2 = \text{PWL}(0\text{s } -10\text{V } 10\text{ms } 10\text{V})$  and  $V_3 = 2\sin(2\pi \times 10^4 t)\text{ V}$ , then obtain a plot of  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_{OUT}$  versus time.

# Differential Amplifier

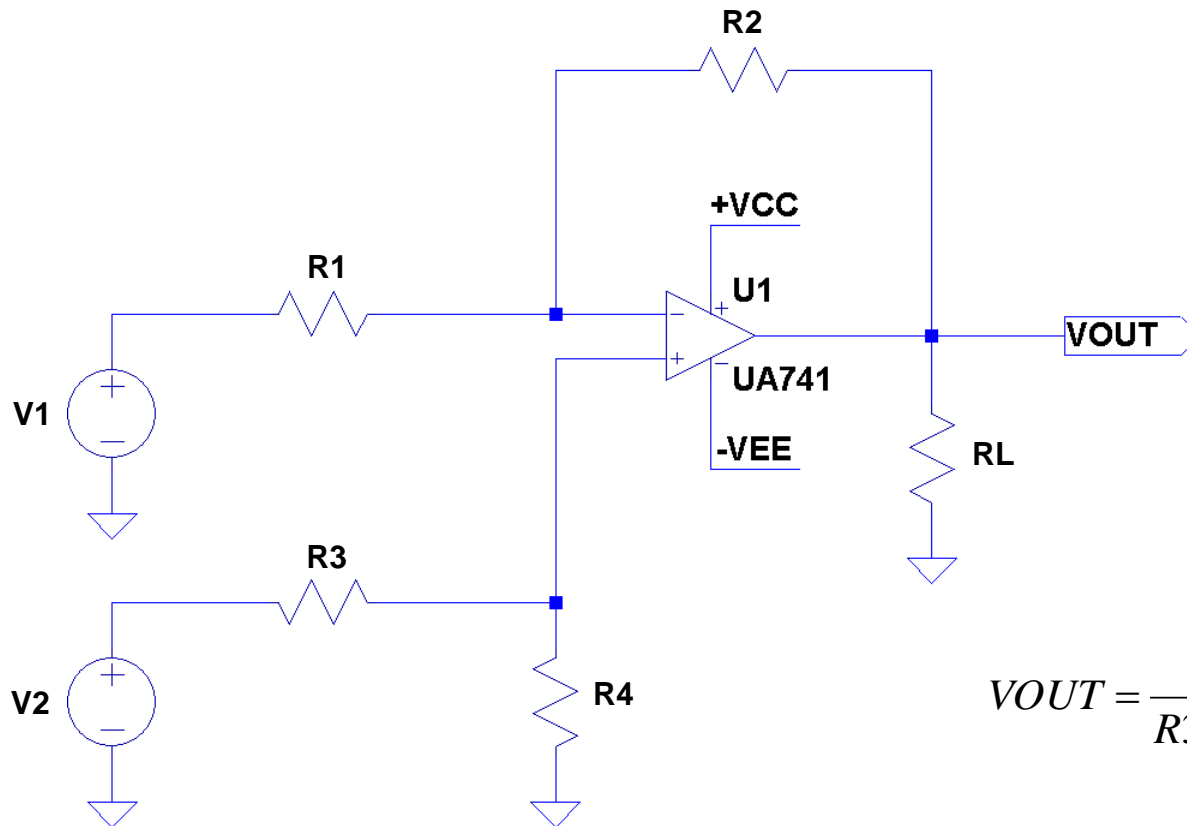

$$V_{OUT} = \frac{R4}{R3 + R4} \left( 1 + \frac{R2}{R1} \right) V2 - \frac{R2}{R1} V1$$



## ***Lab-2: Differential Amplifier***


---

### **❖ Simulation Condition**

- Op Amp:  $\mu A741$
- $R_L = 5\text{ k}\Omega$
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$
- $V_1 = 0.5\sin(2\pi \times 10^4 t)\text{ V}$ ,  $V_2 = 2.5\sin(2\pi \times 10^4 t)\text{ V}$
- Transient analysis from 0 to 1ms

- 1) Determine the values of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  to provide  $V_{OUT} = 3(V_2 - V_1)$ .
- 2) Create the LTSpice schematic of the differential amplifier circuit.
- 3) Obtain a plot of  $V_1$ ,  $V_2$  and  $V_{OUT}$  versus time.
- 4) What is the lowest value of  $R_L$  for maintaining the proper circuit operation.

# Instrumentation Amplifier

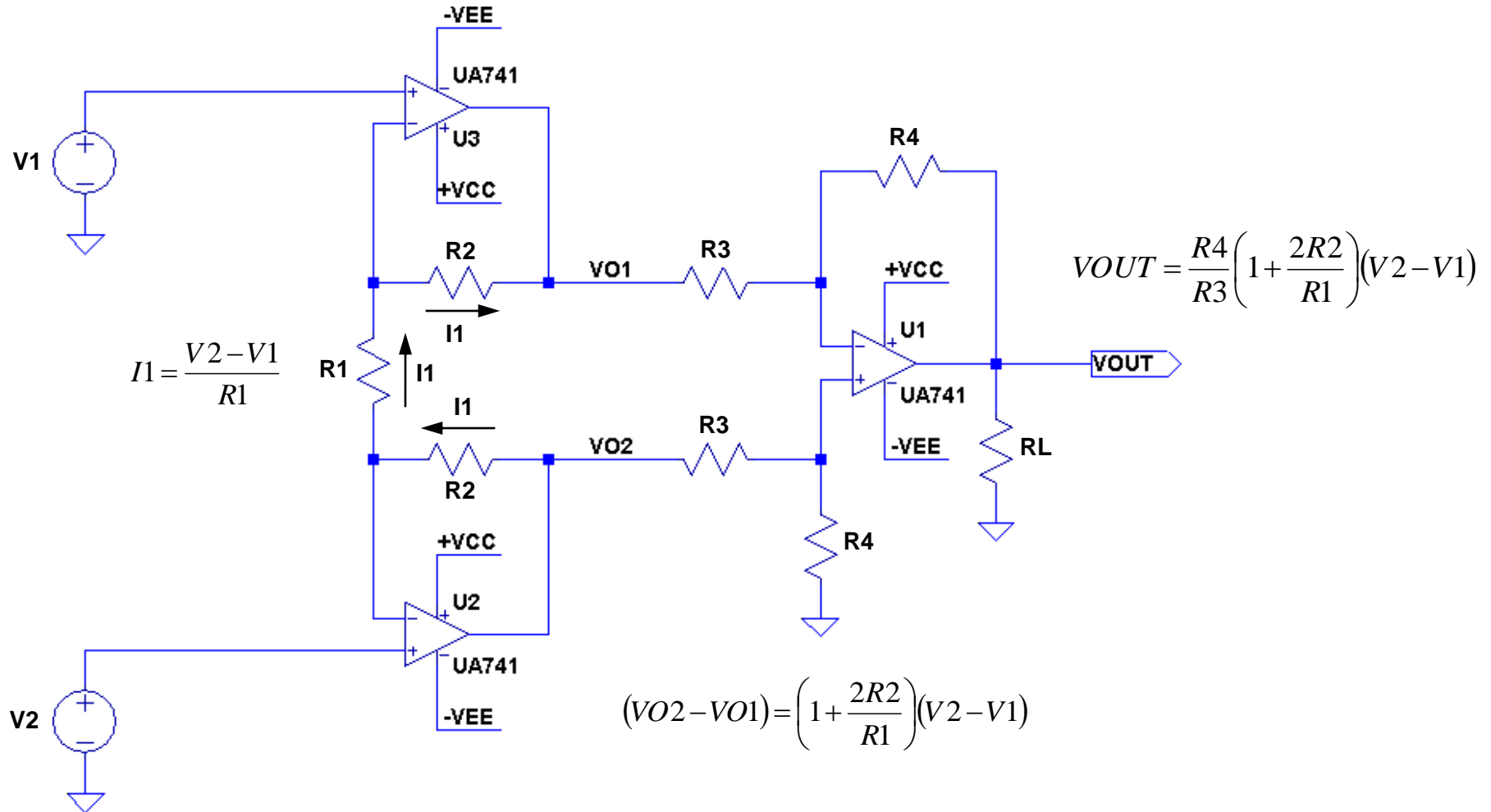



## ***Lab-3: Instrumentation Amplifier***

### **❖ Simulation Condition**

- Op Amp:  $\mu A741$
- $R_L = 5\text{ k}\Omega$
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$
- $V_1 = 1\sin(2\pi \times 10^3 t)\text{ V}$ ,  $V_2 = 2\sin(2\pi \times 10^3 t)\text{ V}$
- Transient analysis from 0 to 10ms

- 1) Determine the values of  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  to provide  $V_{OUT} = 5(V_2 - V_1)$ .
- 2) Create the LTSpice schematic of the instrumentation amplifier circuit.
- 3) Obtain a plot of  $V_1$ ,  $V_2$ ,  $V_{O1}$ ,  $V_{O2}$  and  $V_{OUT}$  versus time.
- 4) Change the input voltage  $V_2$  to  $V_2 = V_P \sin(2\pi \times 10^3 t)\text{ V}$ , then find the highest value of  $V_P$  for maintaining the proper circuit operation.