



# Electronic Circuits Design


---

## *Lecture – 6*


- *Square Waveform Generator*
- *Triangular Waveform Generator*

***Yeonbae Chung***  
***School of Electronics Engineering***  
***Kyungpook National University***

# Square Waveform Generator - 1

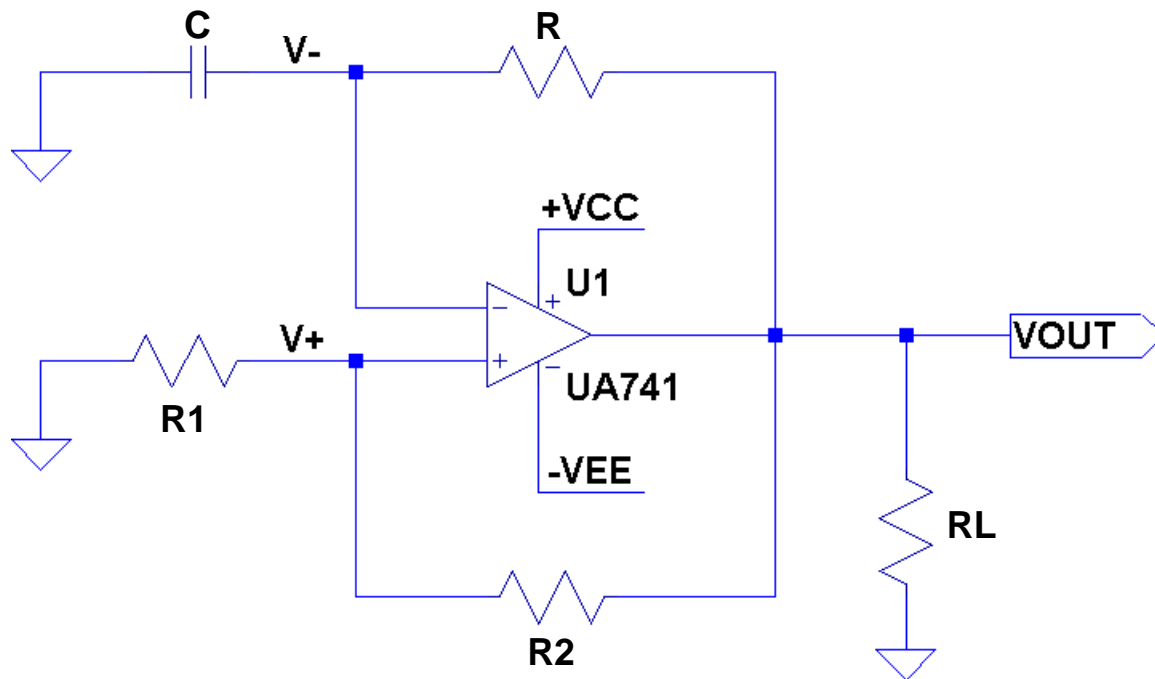

$$\beta = \frac{R1}{R1 + R2}$$

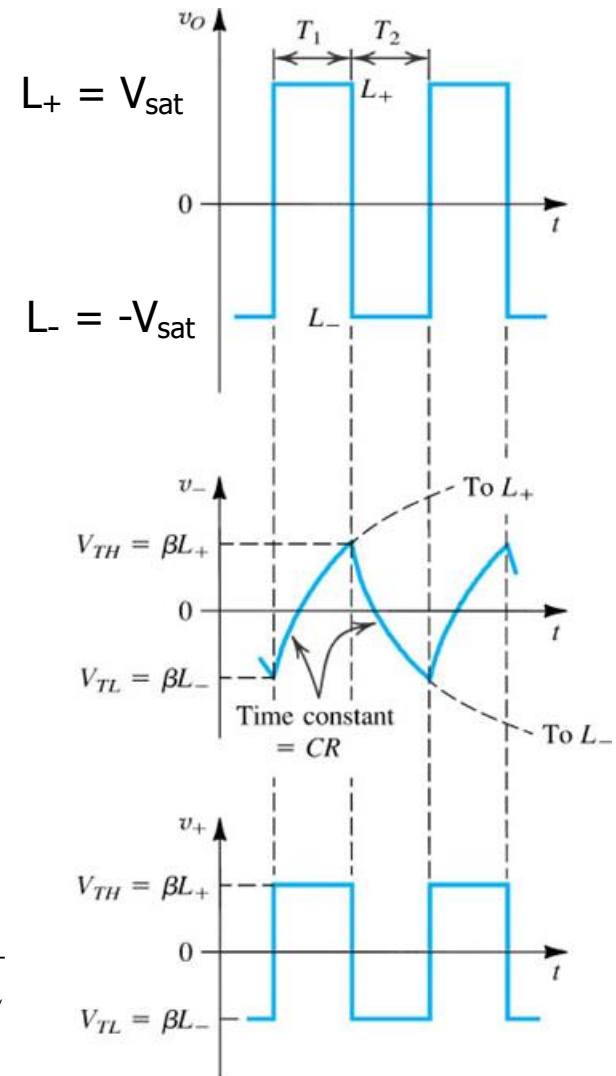

# Square Waveform Generator - 1

- RC charging and discharging voltage:  $v(t) = V_{\infty} - (V_{\infty} - V_{0+})e^{-\frac{t}{RC}}$

- During  $T_1$ :  $\rightarrow$  charging

$$V_- = V_{sat} - (V_{sat} + \beta V_{sat})e^{-\frac{t}{RC}} \Rightarrow T_1 = RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

- During  $T_2$ :  $\rightarrow$  discharging

$$V_- = -V_{sat} - (-V_{sat} - \beta V_{sat})e^{-\frac{t}{RC}} \Rightarrow T_2 = RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

$$\Rightarrow T = T_1 + T_2 = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right) = 2RC \ln\left(\frac{2R_1 + R_2}{R_2}\right)$$

$$\text{If } R_2 = 1.16R_1 \Rightarrow T = 2RC \ln\left(\frac{3.16}{1.16}\right) = 2RC$$

$$f = \frac{1}{T} = \frac{1}{2RC}$$




# ***Lab-1: Square Waveform Generator - 1***

## **❖ Simulation Condition**

- Op Amp:  $\mu A741$**
- $R_L = 5\text{ k}\Omega$**
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$**
- Transient analysis**

- 1) Design the square waveform generator with  $f = 100\text{ Hz}$ , and obtain a plot of  $V_+$ ,  $V_-$  and  $V_{OUT}$  versus time.**
- 2) Design the square waveform generator with  $f = 500\text{ Hz}$ , and obtain a plot of  $V_+$ ,  $V_-$  and  $V_{OUT}$  versus time.**
- 3) Make a comment on your design if you need.**

# Square Waveform Generator - 2

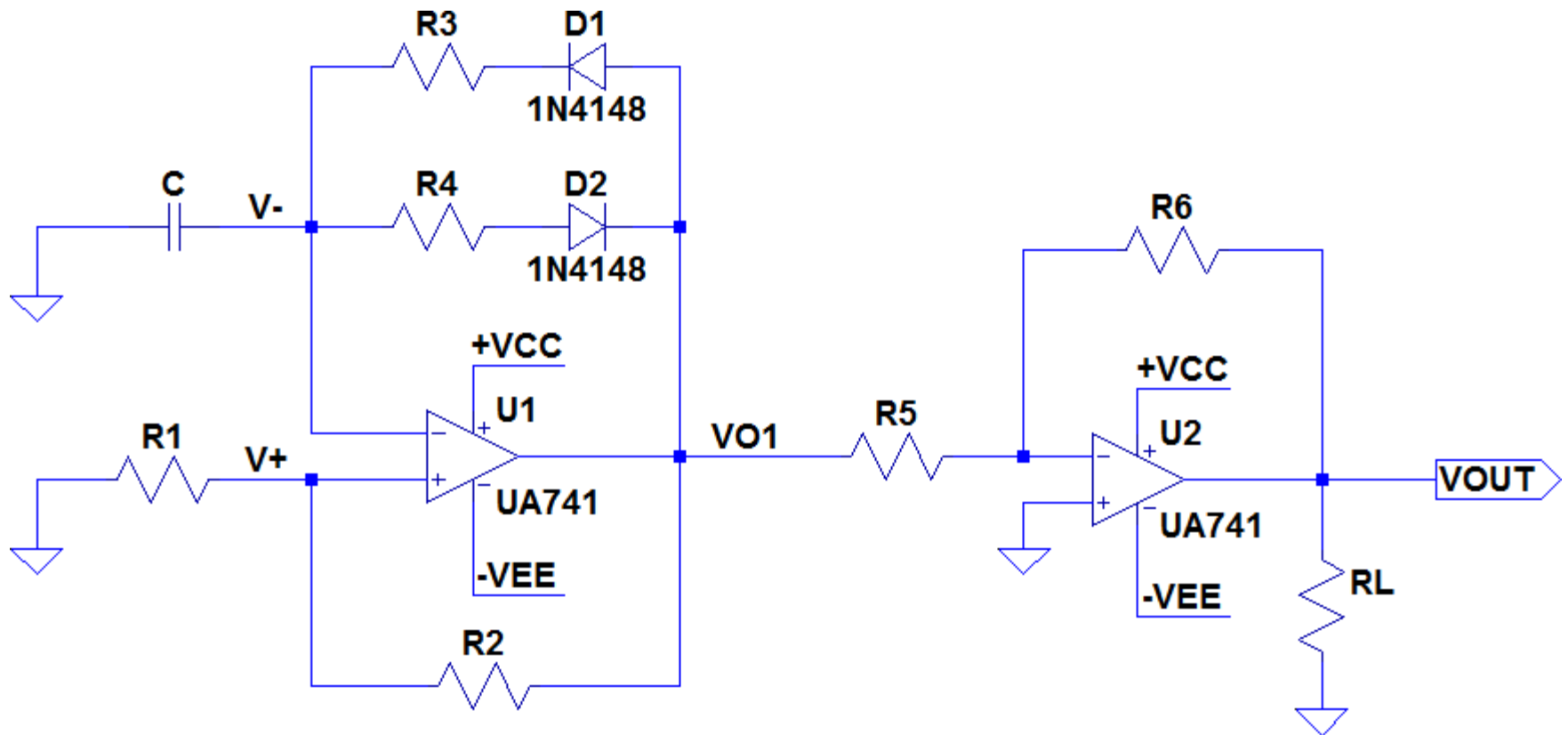




## ***Lab-2: Square Waveform Generator - 2***

### **❖ Simulation Condition**

- Op Amp:  $\mu A741$
- Diode: 1N4148
- $R_L = 5\text{ k}\Omega$
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$
- Transient analysis 0 to 10ms

- 1) Design the square waveform generator whose clock frequency is 1 kHz with 6-V peak-to-peak and 60 % duty cycle. Obtain a plot of  $V_+$ ,  $V_-$ ,  $VO1$  and  $VOUT$  versus time.
- 2) Design the square waveform generator whose clock frequency is 1 kHz with 6-V peak-to-peak and 25 % duty cycle . Obtain a plot of  $V_+$ ,  $V_-$ ,  $VO1$  and  $VOUT$  versus time.
- 3) Make a comment on your design if you need.

# Triangular Waveform Generator

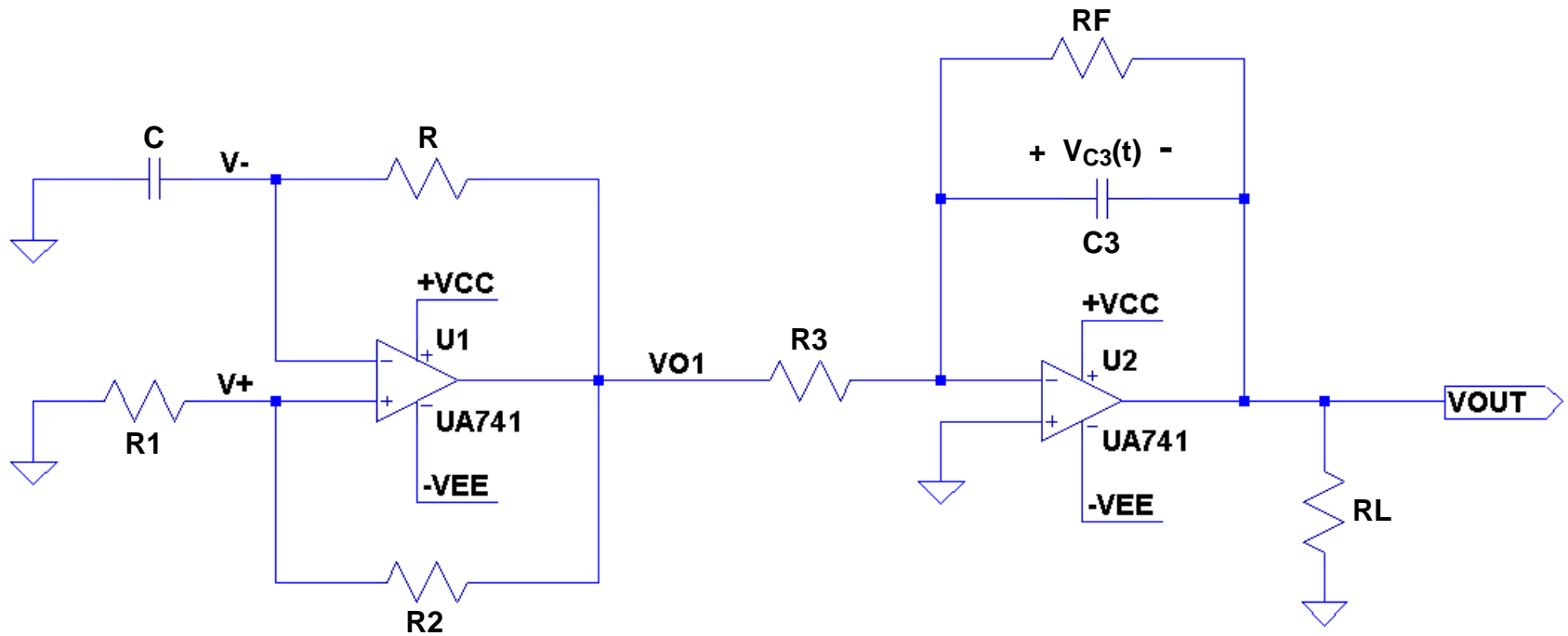

$$V_{OUT} \cong -\frac{1}{R_3 C_3} \int_0^t V_{O1}(t) dt - V_{C3}(t=0)$$



## ***Lab-3: Triangular Waveform Generator***

---

### **❖ Simulation Condition**

- Op Amp:  $\mu A741$
- $R_L = 5\text{ k}\Omega$ ,  $R_F = 200\text{ k}\Omega$
- $+V_{CC} = 15\text{ V}$ ,  $-V_{EE} = -15\text{ V}$
- Transient analysis 0 to 16ms

- 1) Design the triangular waveform generator to provide  $V_{OUT}$  of a symmetrical triangular wave of 18-V peak-to-peak, 0 average, and 1ms-period after  $t = 8\text{ms}$ .
- 2) Obtain a plot of  $V_+$ ,  $V_-$ ,  $V_{O1}$  and  $V_{OUT}$  versus time.
- 3) Make a comment on your design if you need.